Search...

Aptitude Engineering Mathematics Discrete Mathematics Operating System DB Sign In

# Difference between Multiplexer and Demultiplexer

Last Updated: 20 Dec, 2024

A Multiplexer (MUX) and a Demultiplexer (DEMUX) are essential digital circuits in communication systems, performing opposite functions. A multiplexer combines multiple input signals into a single output, while a demultiplexer takes a single input signal and routes it to one of many output lines.

In this article, we'll explore the differences between a multiplexer and a demultiplexer, their advantages, disadvantages, and applications.

## What is a Multiplexer?


A **multiplexer** is a <u>combinational circuit</u> with multiple data inputs and a single output, determined by control or select lines. Often referred to as **MUX**, it requires log2(N)log2(N) selection lines for NN input lines, or equivalently, nn selection lines for 2n2n input lines.

Multiplexers are also known as:

- N-to-1 selectors
- Parallel-to-serial converters
- Many-to-one circuits
- Universal logic circuits

They are mainly used to increase the amount of data that can be sent over a network within a certain amount of time and bandwidth

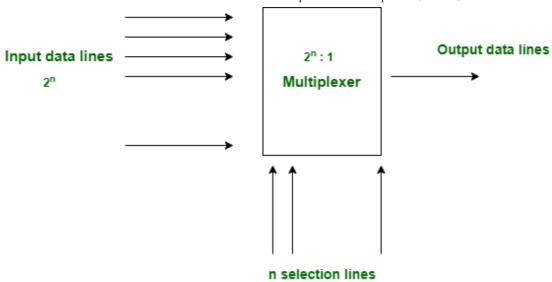Below is the Block Diagram of the Multiplexer, It will have 2<sup>n</sup> Input lines and will select output based on the Select line.



#### Advantages of Multiplexer(MUX)

- Reduces the number of data lines: MUX allows multiple signals to share a single communication line, saving space and resources.
- **Simpler Design**: It simplifies the system by reducing the number of data channels needed.
- **Efficient Use of Resources**: MUX optimizes the use of communication channels or buses.
- Flexible Design: MUX can be used for different types of data and communication formats.
- **Compact Systems**: It helps make systems smaller and simpler by reducing the number of connections.
- Reduces Errors: Fewer data lines mean less chance of interference or noise.

## Disadvantages of Multiplexer(MUX)


- **Complex Control**: It needs extra circuits to select which input is sent, making the design more complicated.
- **Limited Inputs**: The number of inputs depends on the number of control lines (e.g., 2 control lines allow only 4 inputs).
- Propagation Delay: Switching between inputs can introduce delays in high-speed systems.
- **Higher Power Use**: Larger multiplexers with more inputs can consume more power.

• **Signal Loss**: Some signal degradation may occur when combining multiple signals.
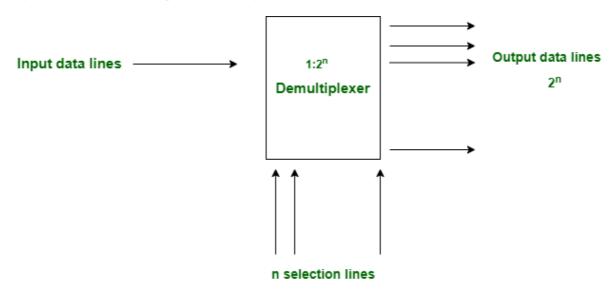
## What is Demultiplexer (DEMUX)?

Demultiplexer is the opposite of multiplexer. It is also termed as DEMUX. It takes input from one source and also converts the data to transmit towards various sources. The demultiplexer has one data input line. The demultiplexer has several control lines (also known as select lines). These lines determine to which output the input data should be sent. The number of control lines determines the number of output lines.

Given below is the block diagram of the Demultiplexer, It will have one Input line and will give  $2^n$  output lines.



### Advantages of Demultiplexers (DEMUX)

- 1. **Efficient Data Distribution**: Routes one input signal to multiple outputs effectively.
- 2. **Reduced Transmission Complexity**: Simplifies transmitter design by minimizing input lines.
- 3. **High-Speed Data Splitting**: Ideal for applications requiring rapid data distribution.
- 4. **Scalability**: Can handle more outputs by increasing control lines.
- 5. **Versatility**: Widely used in TV broadcasting, communication networks, and more.

#### Disadvantages of Demultiplexers (DEMUX)

- 1. **Control Complexity**: Additional circuits are needed for output selection.
- 2. **Limited Outputs**: The number of outputs depends on available control lines.
- 3. **Propagation Delay**: Routing input to outputs may introduce delays in larger systems.
- 4. **Signal Degradation**: Signal strength may reduce when split into multiple outputs.
- 5. **Higher Power Consumption**: Power usage increases with additional outputs.
- 6. Noise Susceptibility: Splitting signals can lead to interference

## Difference Between of Multiplexer and Demultiplexer

Multiplexer(MUX)	Demultiplexer(DEMUX)
Multiplexer processes the digital information from various sources into a single source.	Demultiplexer receives digital information from a single source and converts it into several sources
It is known as Data Selector	It is known as Data Distributor
Multiplexer is a digital switch	Demultiplexer is a digital circuit
It follows combinational logic type	It also follows <u>combinational logic type</u>
It has 2 <sup>n</sup> input data lines	It has single input line
It has a single output data line.	It has 2 <sup>n</sup> output data lines
Efficiently uses bandwidth by combining many signals into a single line for transmission.	Divides a single signal into several parts, so bandwidth is less efficiently used.

Multiplexer(MUX)	Demultiplexer(DEMUX)
Needs control lines to select which input signal to send to the output.	Needs control lines to determine which output line should receive the input signal.
It works on many to one operational principle	It works on one to many operational principle.
May consume more power due to the need for control logic and multiple input connections.	Typically uses less power, especially when splitting a single signal to multiple destinations.
In <u>time division Multiplexing</u> , multiplexer is used at the transmitter end.	In time division Multiplexing, demultiplexer is used at the receiver end.

#### Conclusion

In summary, a **multiplexer** combines multiple signals for efficient data transmission, while a **demultiplexer** splits a single signal for distribution. Both circuits have unique advantages and disadvantages, with their use depending on system requirements like speed, cost, and simplicity.



## **Similar Reads**

## Difference between Multiplexer and Decoder

Both the multiplexer and the decoder operate together to generate signal and data output for various communication and operating channels....